

Lab: Extra Credit Three Way Switch

Name _____ Period _____

PURPOSE: To wire a *real* three way switch circuit after having learned to do one with open knife switches.

PROCEDURE: Using Two Single Pole, Double Throw *Commercial* Switches, a battery, and a light, wire up a *real* three way circuit and test it. **Have the Boom check it off.**

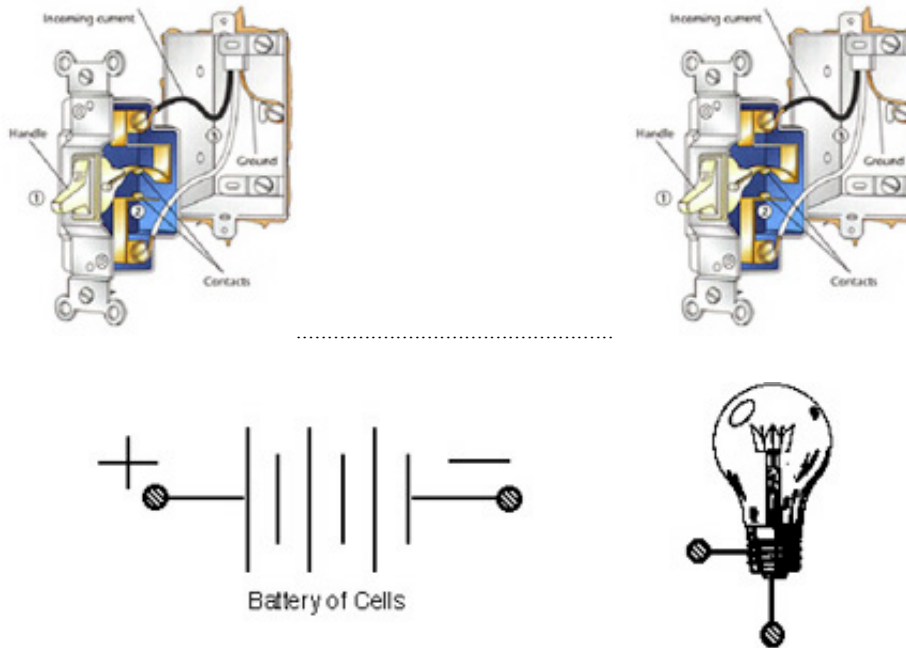


Diagram and Critique: